



ALTERNATING CURRENT

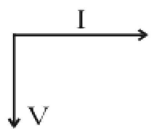
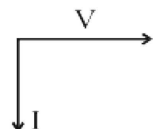
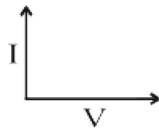
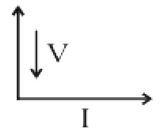
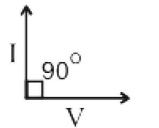
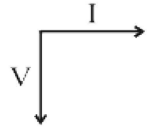

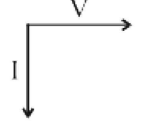
Each question has four possible answers, tick (✓) the correct answer:

- Alternating current is one which changes in a:
 - Magnitude
 - Direction
 - Magnitude as well as direction
 - None of the above
- If V_{rms} be the root mean square value of emf then its peak to peak value is given by:
 - $\frac{V_{\text{rms}}}{\sqrt{2}}$
 - $\sqrt{2} V_{\text{rms}}$
 - $\frac{2}{\sqrt{2} V_{\text{rms}}}$
 - $\frac{V_{\text{rms}}}{2}$
- If I_0 is the peak value of current, then its root mean square value is given by:
 - $\sqrt{2} I_0$
 - $2 I_0$
 - I_0
 - $0.7 I_0$
- A.C can be measure with the help of:
 - Ammeter (D.C)
 - Moving coil galvanometer
 - Hot wire ammeter
 - All of the above
- For a sine wave, the form factor is given by:
 - $\frac{\pi}{2\sqrt{2}}$
 - $\frac{\pi}{2}$
 - $\sqrt{2} \pi$
 - $2\sqrt{2} \pi$
- Alternating current is converted to direct current by:
 - Dynamo
 - Motor
 - Transformer
 - Rectifier
- The out put voltage of an A.C at any time is given by:
 - $V = V_0 \sin \omega t$
 - $V = V_0 \cos \frac{2\pi}{T} \times t$
 - $V = V_0 \sin \frac{2\pi}{T} \times t$
 - None of the above
- The value of capacitive reactance is given by:
 - $X_c = VI$
 - $X_c = \frac{V}{I}$
 - $X_c = \frac{I}{V}$
 - All of above

9. The time during which the voltage sources changes its polarity once is called:
- (a) Time period (b) Critical time
(c) Period of the AC (d) None of the above
10. The SI unit of reactance is:
- (a) ohm (b) Volt – m⁻¹
(c) Volt (d) Ampere
11. Alternating current or emf measuring instruments measures its:
- (a) r.m.s. value (b) Peak value
(c) Average value (d) None of the above
12. The average value of A.C over a complete cycle is:
- (a) I_0 (b) $\frac{I}{\sqrt{2}}$
(c) I (d) None of the above
13. One complete set of positive and negative value of alternating quantities is called:
- (a) Frequency (b) Time period
(c) Amplitude (d) Cycle
14. Reactance offered by a coil having no resistance in a.c circuit is equal to:
- (a) $\frac{1}{\omega L}$ (b) ωL
(c) $\omega^2 L^2$ (d) ωLR
15. Alternating voltage is:
- (a) Varies inversely with time (b) Varies directly with time
(c) Independent of time (d) Varies sinusoidally with time
16. The alternating current can be transmitted:
- (a) Very low cost (b) To very high cost
(c) Long distances (d) Both (a) and (c)
17. Alternating current is produced by a voltage source which polarity:
- (a) Keeps on reversing with time (b) Remains the same
(c) Reverses after period T (d) None of these
18. The output V of an A.C generator at any instant is given by:
- (a) $V = V_0 \sin \omega t$ (b) $V = V_0 \sin \frac{2\pi}{T} t$
(c) $V = V_0 \sin \frac{2\pi}{T} t$ (d) Both (a) and (c)

19. Using $\theta = \omega t$ and $\omega = \frac{2\pi}{T}$, the angle through which the coil of the A.C generator rotates when $t = \frac{T}{2}$ is:
- (a) π (b) Zero
(c) $\frac{\pi}{2}$ (d) 2π
20. If $V = V_o \sin \omega t$ and $\omega = \frac{2\pi}{T}$, the value of alternating voltage V when $t = \frac{3T}{4}$ is:
- (a) $-V_o$ (b) V_o
(c) $V_o = 0$ (d) None of these
21. The waveform of alternating voltage is the graph between:
- (a) Current and time (b) Voltage and time
(c) Voltage and current (d) Voltage along y-axis and time along x-axis
22. The waveform of alternating voltage is a:
- (a) Square (b) Sinusoidal
(c) Rectangular (d) None of these
23. The peak to peak value of alternating voltage is:
- (a) $2V_o$ (b) V_o
(c) $\frac{V_o}{2}$ (d) None of these
24. The average value of alternating voltage over a complete cycle is:
- (a) Zero (b) $0.7 V_{\max}$
(c) $0.707 V_{\max}$ (d) None of these
25. The RMS value of alternating voltage is:
- (a) 0.5 times the peak value (b) 0.7 times the peak value
(c) 0.7 times the instantaneous value (d) Equal to maximum voltage
26. The alternating voltage or current is actually measured by:
- (a) Its RMS value (b) Square root of its mean square value
(c) Peak value (d) Instantaneous value
27. The magnitude of alternating voltage is:
- (a) Always decreases (b) Always increases
(c) Always remains the same (d) Does not remain the same
28. The basic circuit element in a D.C circuit is:
- (a) An inductor (b) A resistor
(c) A capacitor (d) None of these

29. The basic circuit elements in A.C circuits are:
- (a) Thermistor (b) Inductor and resistors
(c) Inductor and capacitor (d) All of above
30. The maximum current I_o passing through a resistance R connected with an alternating voltage source V_o is given by:
- (a) $I_o = R \times V_o$ (b) $I_o = \frac{V_o}{R}$
(c) $I_o = \frac{R}{V_o}$ (d) $I_o = V_o \times R$
31. In a resistive A.C circuit, instantaneous values of voltage and current are:
- (a) In phase (b) Out of phase
(c) Lead each other (d) None of these
32. The dimensions, of R.C matches with:
- (a) $\frac{R}{L}$ (b) $\frac{L}{R}$
(c) RL (d) None of these
33. At what frequency 1 henry inductance offer same impedance as 1 μF capacitor:
- (a) 450 Hz (b) 512 Hz
(c) 1 KHz (d) 159 Hz
34. A transformer has $\frac{N_2}{N_1} = 10$, the load current is 1.0A, the current in primary is:
- (a) 1 A (b) 0.1 A
(c) 11 A (d) 10 A
35. For resistance, \vec{V} and \vec{I} vectors are drawn:
- (a) Parallel to each other (b) Perpendicular to each other
(c) Such that \vec{V} leads \vec{I} (d) None of these
36. When voltage V and current I are in phase the power is expressed as:
- (a) $P = VI \sin \theta$ (b) $P = I^2 R$
(c) $P = VR$ (d) $P = VI \cos \theta$
37. When A.C voltage source is connected to a capacitor:
- (a) Voltage V lags behind current I (b) Current I leads the voltage V
(c) Voltage leads the current I (d) Both (a) and (b)
38. The measure of the opposition offered by a capacitor to the flow of A.C is called:
- (a) Reactance (b) Resistance
(c) Impedance (d) Capacitance

39. Energy in an inductance coil is stored in the form of:
- (a) Electrical energy (b) Light energy
(c) Magnetic energy (d) Heat energy
40. The reactance is the ratio of:
- (a) $V_{\text{rms}}/I_{\text{rms}}$ (b) $V_{\text{rms}} \times I_{\text{rms}}$
(c) $I_{\text{rms}}/V_{\text{rms}}$ (d) $V_{\text{max}} \times V_{\text{rms}}$
41. In case of capacitor, the unit of reactance is:
- (a) Farad (b) Ohm
(c) Newton (d) All of these
42. The reactance of a coil depends upon:
- (a) Inductance of the coil (b) Capacitance of the coil
(c) Thickness of the coil (d) None of these
43. To maintain the current in an inductor, the applied alternating voltage must be:
- (a) Smaller than back emf (b) Greater than back emf
(c) Equal to back emf (d) None of these
44. When A.C voltage is applied to an inductor, the:
- (a) Voltage V leads current I by 90° (b) Voltage V leads current I by 270°
(c) Voltage V leads current I by 0° (d) None of these
45. The phase diagram for an inductor can be shown as:
- (a)  (b) 
(c)  (d) 
46. The phase diagram for a capacitor can be shown as:
- (a)  (b) 
(c)  (d) 
47. If frequency f is in Hz and inductance L is in milli henry, then X_L is in:
- (a) milli ohm (b) kilo ohm
(c) ohm (d) none of these
48. If frequency f is in Hz and capacitance C is in μF then the unit of X_C is:
- (a) Mega ohm (b) Milli ohm
(c) μ ohm (d) None of these

49. Alternating current can be produced by:
- (a) Electric motor (b) Generator
(c) Turbine (d) Transformer
50. Which of the following statement is correct for an A.C circuit:
- (a) The current depends upon the components connected in circuit
(b) The current lags the voltage by a phase angle of 90°
(c) The current leads the voltage by a phase angle of 90°
(d) The current and voltage are in same phase
51. Impedance is the combined effect of:
- (a) Resistance and inductance (b) Resistance and reactance
(c) Inductance and capacitance (d) None of these
52. The unit of impedance is:
- (a) Farad (b) Henry
(c) Tesla (d) Ohm
53. In an RLC circuit, the impedance is:
- (a) Combined effect of resistance and reactance
(b) Another name of resistance
(c) Another name of inductance and capacitance
(d) None of these
54. The amplitude of the effective current is:
- (a) $I_{\text{rms}} \cos \theta$ (b) $I_{\text{rms}} \sin \theta$
(c) $I_0 \cos \theta$ (d) Infinity
55. The graph between time and voltage is:
- (a) tan curve (b) Curved line
(c) Sine curve (d) Straight line
56. Alternating current can be measured by D.C ammeter because if:
- (a) A.C is virtual (b) Average current for complete cycle is zero
(c) A.C cannot pass through D.C ammeter (d) None of the above
57. The highest value reached by the voltage or current in one cycle is known as:
- (a) Peak value (b) Minimum value
(c) Average value (d) Zero value
58. Inductive reactance ωL of a coil is expressed in:
- (a) Ohm (b) Ampere
(c) Volt (d) None of the above
59. The current flows from $0 \rightarrow T/2$ is:
- (a) + ve direction of A.C (b) - ve direction of A.C
(c) Towards zero (d) None of the above

60. The current flows from $T/2 \rightarrow T$ is:
- (a) – ve direction of A.C (b) + ve direction of A.C
(c) Towards zero (d) All of the above
61. The most common source of A.C voltage is:
- (a) Cell (b) A.C generator
(c) A.C transformer (d) Motor
62. Voltage drop in A.C circuit is the product of current and:
- (a) Impedance (b) Inductance
(c) Resistance (d) None of the above
63. In a purely capacitive A.C circuit, the current is:
- (a) In phase with emf (b) The emf by 90°
(c) Leads the emf by 90° (d) All of the above
64. With high frequencies, capacitive reactance:
- (a) Remain unchanged (b) Increases
(c) Decreases (d) None of the above
65. With increase of frequency of A.C supply, the inductive reactance is:
- (a) Decreases (b) Increases as square of frequency
(c) Remain unchanged (d) Increases as directly to frequency
66. The natural frequency of L.C circuit is equal to:
- (a) $\frac{1}{2\pi} \sqrt{\frac{C}{L}}$ (b) $\frac{1}{2\pi} \sqrt{\frac{L}{C}}$
(c) $\frac{1}{2\pi\sqrt{LC}}$ (d) $\frac{\sqrt{LC}}{2\pi}$
67. With increase in frequency of an A.C supply, the impedance of LCR series circuit:
- (a) Decrease (b) Increases
(c) Remains constant (d) First decrease, becomes minimum and then increase
68. SI The unit of impedance is:
- (a) Hertz (b) Henry
(c) Volt (d) Ohm
69. An expression for impedance for R.C series circuit is given by:
- (a) $Z = \sqrt{R^2 + \frac{1}{\omega c}}$ (b) $Z = \sqrt{R + \frac{1}{\omega c}}$
(c) $Z = \sqrt{R^2 + \left(\frac{1}{\omega c}\right)^2}$ (d) $Z = \sqrt{\left(R + \frac{1}{\omega c}\right)^2}$

70. The phase angle θ in an R.C series circuit is expressed as:
- (a) $\theta = \cos^{-1} \left(\frac{I}{\omega CR} \right)$ (b) $\theta = \tan \left(\frac{1}{\omega CR} \right)$
- (c) $\theta = \tan^{-1} \left(\frac{X_C}{R} \right)$ (d) None of these
71. The phase angle θ in an R.L series circuit is expressed as:
- (a) $\theta = \tan^{-1} \left(\frac{\omega L}{R} \right)$ (b) $\theta = \tan \left(\frac{\omega L}{R} \right)$
- (c) $\theta = \tan^{-1} \left(\frac{R}{\omega L} \right)$ (d) None of these
72. The impedance Z of an R.L series circuit is expressed as:
- (a) $Z = \sqrt{(\omega L)^2 + \frac{1}{R^2}}$ (b) $Z = \sqrt{R^2 + (\omega L)^2}$
- (c) $Z = \sqrt{R^2 + \left(\frac{1}{\omega L} \right)^2}$ (d) None of these
73. In an R.L.C series circuit, the quantities which are directed opposite to each other are:
- (a) X_C and R (b) X_C and X_L
- (c) X_C and L (d) X_L and C
74. The condition of resonance in an R.L.C series circuit is that:
- (a) $X_L = X_C$ (b) $X_L > X_C$
- (c) $X_L < X_C$ (d) None of these
75. The equation which satisfied the resonance condition is:
- (a) $X_L = X_C$ (b) $\omega = \frac{1}{\sqrt{LC}}$
- (c) $f = \frac{1}{2\pi\sqrt{LC}}$ (d) All of above
76. Power factor is defined by:
- (a) $\cos \theta$ (b) $\sin \theta$
- (c) $\tan \theta$ (d) $\sec \theta$
77. At resonance frequency, the impedance of an R.L.C series circuit is:
- (a) Minimum (b) Zero
- (c) Maximum (d) None of these
78. At resonance frequency in an R.L.C series circuit, V_L and V_C :
- (a) Greater than the source voltage (b) Smaller than the source voltage
- (c) Equal to source voltage (d) None of these
79. A.C voltmeter measures:
- (a) Peak value (b) Average voltage
- (c) Peak inverse voltage (d) r.m.s voltage

80. The impedance of pure anti-resonant which at resonance is:
- (a) 0 (b) $\frac{1}{2}$
(c) 1 (d) ∞
81. The positive value of current and voltage over a cycle is:
- (a) Positive (b) Zero
(c) Negative (d) None of the above
82. A capacitor is a perfect insulator for:
- (a) Direct current (b) Alternating current
(c) Both (a) and (b) (d) None of above
83. In comparison to D.C transmission losses in A.C are:
- (a) Low (b) High
(c) Negligible (d) None of the above
84. In A.C circuits, the A.C instruments indicate:
- (a) Peak values (b) Square of peak values
(c) Square root of peak values (d) Virtual values
85. When resistance is increased in a series LCR circuit:
- (a) Impedance decreases (b) Reactance increases
(c) Phase angle increases (d) phase angle decreases
86. In an L.C.R, A.C circuit, the current becomes minimum when:
- (a) $X_L > X_C$ (b) $X_L = X_C$
(c) $\sqrt{X_L X_C} = 1$ (d) $X_L < X_C$
87. The resonance frequency in case of series resonance circuit is given by:
- (a) $f = \frac{1}{4\pi\sqrt{LC}}$ (b) $f = \frac{1}{2\pi\sqrt{L C}}$
(c) $f = \frac{1}{5\pi\sqrt{L C}}$ (d) None of the above
88. Which current can pass through a capacitor continuously:
- (a) Direct current (b) Electronic current
(c) Alternating current (d) Both (a) and (b)
89. An inductor may store energy in its:
- (a) Magnetic field (b) Electric field
(c) Coil (d) None of the above
90. The reactance of inductor depends upon:
- (a) L (b) ωL
(c) ω (d) All of the above

91. A device that allows only the continuous flow of AC through a circuit is:
(a) Capacitor (b) Inductor
(c) Dynamo (d) D.C motor
92. A.C varies as function of:
(a) Time (b) Voltage
(c) Current (d) Displacement
93. In electromagnetic waves, the electric and magnetic fields are:
(a) Perpendicular (b) Parallel
(c) Antiparallel (d) At an angle of 45°
94. The impedance of a series circuit containing capacitance C, inductance L and resistance R is:
(a) $R + L - \frac{1}{C}$ (b) $\frac{1}{R} + L - C$
(c) $R + L + C$ (d) None of the above
95. The effective value of any sinusoidal alternating current or voltage is:
(a) $\sqrt{3}$ times its maximum value (b) $\frac{1}{\sqrt{2}}$ times its maximum value
(c) $\sqrt{2}$ times its maximum value (d) None of the above
96. In modulation, low frequency signal is known as:
(a) Loaded signal (b) Fluctuated signal
(c) Harmonic signal (d) Modulation signal
97. As a result of modulation, the resultant wave is known as:
(a) Energetic carriers wave (b) Carrier wave
(c) Modulated carrier wave (d) None of the above
98. The reactance X_C for a capacitor across an alternating source of frequency is:
(a) $X_c = \frac{f}{2\pi c}$ (b) $X_c = 2\pi f c$
(c) $X_c = \frac{f c}{2\pi}$ (d) $X_c = \frac{1}{2\pi f c}$
99. In A.C circuits, current and voltage is controlled by:
(a) Inductor L (b) Resistance R
(c) Capacitance C (d) All of the above
100. A pure inductive coil is that which has:
(a) No impedance (b) No ohmic resistance
(c) Some ohmic resistance (d) None of these
101. If X be the reactance, Z be impedance then in a series L.C.R circuit:
(a) $X^2 = (Z + R)^2$ (b) $X^2 = (Z - R)^2$
(c) $X^2 = Z^2 - R^2$ (d) $X^2 = Z^2 + R^2$

102. In a series L.C.R circuit, the total reactance of the circuit is:
- (a) $(X_L - X_C)^2$ (b) $\sqrt{X_L^2 - X_C^2}$
(c) $X_L + X_C$ (d) $\sqrt{(X_L - X_C)^2}$
103. Electrical resonance in an LCR A.C circuit is very sharp if:
- (a) R is large (b) R is small
(c) $R = X_L$ or X_C (d) None of these
104. The instantaneous voltage across a pure inductance is:
- (a) In phase with current (b) Lags the current by 90°
(c) Leads the current by 90° in phase (d) None of these
105. The process of combining low frequency signal with high frequency radio waves is called:
- (a) Resonance (b) Fluctuation
(c) Modulation (d) Amplitude
106. For parallel resonant circuit, the resonance current is:
- (a) Zero (b) Minimum
(c) Maximum (d) One
107. In L.C parallel circuit, the coil draws:
- (a) Leading current (b) Lagging voltage
(c) Lagging current (d) Leading voltage
108. The reciprocal of impedance is called:
- (a) Admittance (b) Capacitance
(c) Inductance (d) Resistance
109. The circuit in which current and voltage are in phase, the power factor is:
- (a) Double (b) three times
(c) One (d) Zero
110. Capacity time constant is given by:
- (a) $\frac{1}{RC}$ (b) R/C
(c) RC (d) $\frac{C}{R}$
111. In which of the following, the loss of energy is less:
- (a) Alternating current (b) Direct current
(c) Photo electric current (d) None of the above
112. At high frequency, the current through a capacitor is:
- (a) Small (b) Infinity
(c) Zero (d) Large

113. The reactance of 1 farad capacitance when connected to D.C circuit is:
- (a) Infinite (b) One
(c) Zero (d) None of these
114. Pure choke consumes:
- (a) Minimum power (b) Maximum power
(c) No power (d) Average power
115. Radio frequency choke is:
- (a) Iron cored (b) Air Cored
(c) Air as well as iron cored (d) None of these
116. A choke is preferred to a capacitor to decrease the A.C in a circuit because the capacitor:
- (a) Has power factor $\cos \phi = 1$ (b) May not be a leak proof wattless resistance
(c) Leak proof wattless resistance (d) None of these
117. The peak value of alternating voltage is 423 volts, its rms value is:
- (a) 300 volts (b) 423 volts
(c) 150 volts (d) 211.5 volts
118. The purpose of choke in a fluorescent lamp is:
- (a) Increase the current (b) Decrease the current
(c) Decrease the voltage (d) Increase the voltage
119. The power dissipation in a pure inductive or capacitive circuit is:
- (a) Zero (b) Maximum
(c) Opposite (d) Negative
120. As series resonance in L.C.R circuit, the impedance is equal to:
- (a) Inductive reactance (b) Ohmic resistance
(c) Capacitive reactance (d) None of these
121. The frequency of an A.C may be associated by:
- (a) $f = \frac{IV}{T}$ (b) $f = \frac{I}{T}$
(c) $f = \frac{1}{T}$ (d) None of these
122. The reactance of magnitude X_C of a capacitor joined across a alternating source can be found by a relation:
- (a) $X_C = \frac{V_{rms}}{I_{rms}}$ (b) $X_C = V_{rms} + I_{rms}$
(c) $X_C = \frac{I_{rms}}{V_{rms}}$ (d) None of these

123. The magnitude of r.m.s value of voltage can be expressed as:

(a) $V_{\text{rms}} = \frac{V_o + V}{\sqrt{2}}$

(b) $V_{\text{rms}} = \frac{V_o}{\sqrt{2}}$

(c) $V_{\text{rms}} = \frac{V_o + V_o}{2}$

(d) None of these

124. Modulation is the process of:

(a) Combining low frequency signal with carrier

(b) Separating the low frequency signal from higher frequency radio wave

(c) Combining low frequency signal with high frequency radio waves

(d) Both (a) and (c)

125. For modulation purpose, high frequency radio waves are called:

(a) Carrier waves

(b) Transverse waves

(c) Radio waves

(d) Longitudinal waves

126. The low frequency signal used for modulation is called:

(a) Carrier signal

(b) Radio signal

(c) Modulating signal

(d) None of these

127. The amplitude modulation A.M transmission frequencies range from:

(a) 540 Hz to 1600 Hz

(b) 540 Hz to 1500 MHz

(c) 540 KHz to 1600 KHz

(d) None of these

128. In frequency modulation, the amplitude of carrier waves is:

(a) Increases

(b) Remains constant

(c) Decreases

(d) None of these

129. Modulation is achieved by changing the:

(a) Frequency and amplitude of the carrier waves

(b) Only frequency of the carrier wave

(c) Only amplitude of the carrier wave

(d) None of these

130. If frequency of rotating coil of an A.C. generator is f Hz then frequency of e.m.f. produced is:

(a) 50 Hz

(b) 60 Hz

(c) f Hz

(d) None of these


131. In figure phase at B is:

(a) $\frac{\pi}{2}$

(b) π

(c) $\frac{3\pi}{2}$

(d) 2π

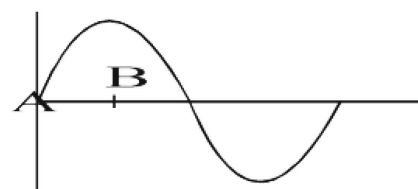

132. The basic circuit element in a D.C. circuit is:

- (a) Capacitor (b) Transistor
(c) Resistor (d) Inductor

133. For $q - t$ graph, slope shows:

- (a) Current (b) Voltage
(c) e.m.f. (d) None of these

134. Slope of a horizontal line is:


- (a) Zero (b) Infinite
(c) Maximum (d) None of these

135. For A.C. through a capacitor, current ——— voltage.

- (a) Lags by $\frac{\pi}{2}$ (b) Leads by $\frac{\pi}{2}$
(c) $\tan^{-1} \frac{1}{\omega CR}$ (d) $\tan^{-1} \frac{\omega^2}{R}$

136. When switch S in closed bulb is:

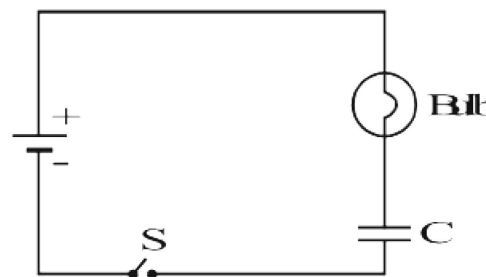- (a) ON
(b) OFF
(c) Both (a), (b)
(d) None of these



137. When A.C. pass through an inductor, voltage leads the current by:

- (a) Half cycle (b) Quarter cycle
(c) Full cycle (d) None of these

138. In case of inductor, in third quarter power is:

- (a) Positive (b) Negative
(c) Both (a), (b) (d) None of these

139. Since an inductor does not consume energy coil is used for controlling A.C. Such a coil is called:

- (a) Resistor (b) Choke
(c) Starter (d) None of these

140. When 10 V are applied to an A.C. circuit, the current flowing in it is 100 mA. Its impedance is:

- (a) 100Ω (b) 200Ω
(c) 10Ω (d) 300Ω

141. In a R-C series circuit, current ——— applied voltage by $\theta =$

- (a) Lead, $\tan^{-1} \frac{1}{\omega CR}$ (b) Lead, $\frac{\pi}{2}$
(c) Lags, $\tan^{-1} \frac{1}{\omega CR}$ (d) Lags, $\frac{\pi}{2}$

142. In a R-L series circuit, current ————— applied voltage by $\theta =$
- (a) Lags, $\frac{\pi}{2}$ (b) Lags, $\tan^{-1} \frac{\omega L}{R}$
- (c) Leads, $\tan^{-1} \frac{\omega L}{R}$ (d) None of these
143. Series resonance circuit is also called:
- (a) R-L-C series circuit (b) Acceptor circuit
- (c) Both (a), (b) (d) None of these
144. The resonance frequency is:
- (a) $\frac{1}{2\pi\sqrt{2LC}}$ (b) $\frac{1}{4\pi\sqrt{LC}}$
- (c) $\frac{0.0159}{\sqrt{LC}}$ (d) None of these
145. Parallel resonance circuit is also called:
- (a) LC parallel (b) Tank
- (c) Rejector (d) All of these
146. At resonance, impedance of parallel resonance circuit is ————— and it is equal to —————.
- (a) Maximum, $\frac{L}{C_r}$ (b) Minimum, $\frac{L}{C_r}$
- (c) Zero (d) None of these
147. For L-C parallel circuit, power factor is:
- (a) Zero (b) One
- (c) Two (d) Three
148. If capacitance of L-C parallel circuit is made four times then $f =$ —————.
- (a) Twice (b) Four times
- (c) One fourth (d) One half
149. A $100 \mu\text{F}$ capacitor will offer a reactance of:
- (a) 60Ω (b) 90Ω
- (c) 32Ω (d) 42Ω
150. If a glass plate is placed between plates of a capacitor, in series with a lighted bulb, the brightness of the bulb.
- (a) Remains same (b) Decreases
- (c) Increases (d) Bulb turns off
151. Three phase supply also provides:
- (a) 230 V (b) 460 V
- (c) 400 V (d) None of these

152. The electromagnetic spectrum contains:
- (a) Radio waves (b) X-rays
(c) Microwaves (d) All of these
153. Who proved that light waves are electromagnetic?
- (a) Faraday (b) Einstein
(c) Maxwell (d) Enderson
154. Formula to prove speed of electromagnetic wave is equal to speed of light is:
- (a) $V = \frac{S}{t}$ (b) $\frac{1}{\sqrt{\epsilon_0 \mu_0}}$
(c) $\sqrt{\frac{\epsilon_0}{\mu_0}}$ (d) $\sqrt{\epsilon_0 \mu_0}$
155. Value of μ_0 is:
- (a) $4\pi \times 10^{-7} \text{ Hm}^{-1}$ (b) $4\pi \times 10^{-7} \text{ wbA}^{-1}\text{m}^{-1}$
(c) $4\pi \times 10^{-7} \text{ wb Am}$ (d) Both (a), (c)
(e) Both (a), (b)
156. A capacitor of capacitance $30 \mu\text{F}$ is charged by a constant current of 10 mA . If initially capacitor is uncharged, what is time taken for potential difference across capacitor to reach 300 V ?
- (a) 0.9 sec. (b) 15 sec.
(c) $1.5 \times 10^{-5} \text{ s}$ (d) $0.9 \times 10^{-3} \text{ s}$

ANSWERS

1.	(c)	2.	(b)	3.	(d)	4.	(c)	5.	(a)
6.	(d)	7.	(a)	8.	(b)	9.	(c)	10.	(a)
11.	(a)	12.	(c)	13.	(d)	14.	(b)	15.	(d)
16.	(d)	17.	(a)	18.	(d)	19.	(a)	20.	(a)
21.	(d)	22.	(b)	23.	(a)	24.	(a)	25.	(b)
26.	(a)	27.	(d)	28.	(b)	29.	(b)	30.	(b)
31.	(a)	32.	(b)	33.	(d)	34.	(d)	35.	(a)
36.	(b)	37.	(d)	38.	(a)	39.	(c)	40.	(a)
41.	(b)	42.	(a)	43.	(c)	44.	(a)	45.	(d)
46.	(a)	47.	(a)	48.	(a)	49.	(b)	50.	(a)
51.	(b)	52.	(d)	53.	(a)	54.	(a)	55.	(c)
56.	(b)	57.	(a)	58.	(a)	59.	(a)	60.	(a)
61.	(b)	62.	(a)	63.	(c)	64.	(d)	65.	(d)
66.	(c)	67.	(d)	68.	(d)	69.	(c)	70.	(c)
71.	(a)	72.	(b)	73.	(b)	74.	(a)	75.	(d)
76.	(a)	77.	(a)	78.	(b)	79.	(d)	80.	(d)
81.	(b)	82.	(a)	83.	(c)	84.	(d)	85.	(d)
86.	(b)	87.	(b)	88.	(c)	89.	(a)	90.	(b)
91.	(a)	92.	(a)	93.	(a)	94.	(d)	95.	(b)
96.	(d)	97.	(c)	98.	(d)	99.	(d)	100.	(b)
101.	(c)	102.	(d)	103.	(b)	104.	(c)	105.	(c)
106.	(b)	107.	(c)	108.	(a)	109.	(c)	110.	(a)
111.	(a)	112.	(d)	113.	(a)	114.	(c)	115.	(b)
116.	(b)	117.	(a)	118.	(b)	119.	(b)	120.	(b)
121.	(c)	122.	(a)	123.	(b)	124.	(d)	125.	(a)
126.	(c)	127.	(c)	128.	(b)	129.	(a)	130.	(c)
131.	(a)	132.	(c)	133.	(a)	134.	(a)	135.	(b)
136.	(b)	137.	(b)	138.	(a)	139.	(b)	140.	(a)
141.	(c)	142.	(c)	143.	(c)	144.	(c)	145.	(d)
146.	(a)	147.	(b)	148.	(d)	149.	(c)	150.	(b)
151.	(c)	152.	(d)	153.	(c)	154.	(b)	155.	(c)
156.	(a)								