



ELECTRONICS

Each question has four possible answers, tick (✓) the correct answer:

1. Temperature coefficient of resistivity of a semi conductor is:
(a) Constant (b) Positive
(c) Negative (d) Variable
2. The pn junction on forward biasing acts as:
(a) Capacitor (b) Low resistor
(c) Inductor (d) High resistor
3. Which one of the following is not semi conductor:
(a) Silicon (b) Copper
(c) Gallium arsenide (d) Germanium
4. The average gap for Germanium at 0K is:
(a) 1.12 eV (b) 0.02 eV
(c) 6.72 eV (d) 7.2 eV
5. The process of doping causes the resistivity of semi conductor to:
(a) Decrease (b) Remains constant
(c) Increase (d) None of these
6. Depletion region has:
(a) Electrons only (b) Holes only
(c) Both electrons and holes (d) Neither holes nor electrons
7. An n-type substance is:
(a) Electrically neutral (b) Negatively charged
(c) Positively charged (d) None of these
8. Holes exist in:
(a) Conductors (b) Semi conductors
(c) Insulators (d) All of the above
9. A pn junction cannot be used as:
(a) A detector (b) A rectifier
(c) An amplifier (d) None of these



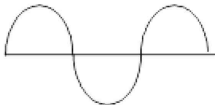

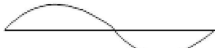







10. Hole is equivalent to:
- (a) A positive charge (b) A negative charge
(c) A neutral (d) None of these
11. There is no current due to holes in good electrical conductors because they have:
- (a) Large forbidden energy gap (b) No valance electron
(c) Overlapping valance & conduction band (d) None of these
12. Silicon is the most commonly used:
- (a) Insulator (b) Semi-conductor
(c) Dielectric (d) Conductor
13. The crystal of Germinium or silicon in its pure form at absolute zero acts as:
- (a) Insulater (b) Conductor
(c) Semi-conductor (d) None of these
14. The crystal of germinium or silicon in its pure form at room temperature acts as:
- (a) Insulator (b) Conductor
(c) Semi-conductor (d) None of these
15. All the valence electrons present in a crystal of silicon are bounded in their orbits by:
- (a) Covalent bond (b) Ionic bond
(c) Molecular bond (d) None of these
16. Majority charge carries in the P-type region of p-n-junction are:
- (a) Protons (b) Electrons
(c) Positrons (d) Holes
17. The impurity in the germinium is usually in the ratio of:
- (a) $1:10^6$ (b) $1:10^4$
(c) $1:10^8$ (d) $1:10^{10}$
18. A potential barrier of 0.7V exists across p-n junction made from:
- (a) Silicon (b) Germinium
(c) Indium (d) Gallium
19. A Potential difference is developed across the depletion region of p-n junction due to:
- (a) Negative ions (b) Positive ions
(c) Both positive and negative ions (d) None of these
20. The external potential difference applied to p-n junction for forward biasing supplied energy to:
- (a) Free electrons in n region (b) Holes in p-region
(c) Both free electrons and holes (d) None of these

21. In forward biased situation, as the biasing voltage is increased, the current:
- (a) Does not change (b) Decreases
(c) Also increases (d) None of these
22. While drawing a graph between current and biasing voltage in p-n junction, the current is taken:
- (a) Along x-axis (b) Along -y-axis
(c) Along x-axis and in mA (d) Along +y-axis
23. In reverse biased, the resistance offered by the p-n junction is of the order of:
- (a) A few $M\Omega$ (b) Several $M\Omega$
(c) A few ohms (d) None of these
24. The semi conductor diode has the property of:
- (a) Two way conduction (b) Zero conduction
(c) One way conduction (d) Amplification
25. Electrons present in P-type material due to thermal pair generation are:
- (a) Majority carriers (b) Minority carriers
(c) Dual carriers (d) None of these
26. Semi conductors with donor atoms and free electrons belong to the type:
- (a) n (b) P
(c) Both n and P (d) Any of above
27. P-n junction when reversed biased acts as a:
- (a) Capacitor (b) Inductor
(c) On switch (d) Off switch
28. In an n-type semi conductor there are:
- (a) Holes as majority carrier (b) Immobile positive ions
(c) Immobile negative ions (d) None of these
29. The width of depletion region of a junction:
- (a) Increase with inverse biasing (b) Decrease with light doping
(c) Increase with heavy doping (d) None of these
30. Which one of the following has the greatest energy gap:
- (a) Conductor (b) Semi conductor
(c) Insulator (d) None of these
31. Which one of the following has smallest energy gap:
- (a) Conductors (b) Semi conductors
(c) Insulators (d) None of these

32. Minority carries in n-type substances are:
- (a) Protons (b) Electrons
(c) Neutrons (d) Holes
33. Minority carriers in a p-type substances are:
- (a) Protons (b) electrons
(c) Neutrons (d) Holes
34. A junction between p and n materials forms:
- (a) An amplifier (b) An oscillator
(c) A detector (d) A semi conductor diode
35. Semi conductor diode conducts only when it is:
- (a) Reverse biased (b) Forward biased
(c) Not biased (d) None of these
36. The forward current through a semi conductor diode circuit is due to:
- (a) Electrons (b) Holes
(c) Majority carriers (d) Minority carriers
37. The reverse current through a semi conductor diode is due to:
- (a) Electrons (b) Holes
(c) Majority carriers (d) Minority carriers
38. In pn junction, p-type end is basically referred as:
- (a) Anode (b) Cathode
(c) Neutral (d) None of these
39. In half wave rectification, the output DC voltage is obtained across the load for:
- (a) The negative half cycle of input AC (b) The positive half cycle of input AC
(c) Both the input of AC (d) None of the above
40. In full wave rectification, the output DC voltage is obtained across the load for:
- (a) The positive half cycle of input AC (b) The negative half cycle of input AC
(c) Complete cycle of input AC (d) None of these
41. Forward resistance of p-n junction is:
- (a) Few ohms (b) Mega ohms
(c) Infinity (d) Kilo ohms
42. Reverse resistance of p-n junction is:
- (a) Low (b) Zero
(c) Very high (d) None of these




43. Conversion of alternating current into direct current is called:
- (a) Modulation (b) Amplification
(c) Oscillation (d) Rectification
44. A region having zero charge particle:
- (a) Depletion region (b) Potential difference
(c) Curved region (d) None of above
45. The potential difference across depletion region in case of Si is:
- (a) 0.6 volt (b) 0.9 volt
(c) 0.7 volt (d) 0.2 volt
46. The potential difference across depletion region in case of Ge is:
- (a) 0.3 volt (b) 0.7 volt
(c) 0.6 volt (d) 0.8 volt
47. The most commonly used diode for special purpose is:
- (a) Light emitting diode (b) Photo diode
(c) Photo voltaic cell (d) All of above
48. A light emitting diode is made from:
- (a) Germinium (b) Silicon
(c) Gallium arsenide (d) Phosphorus
49. The number of LEDs required to display all the digits is:
- (a) Seven (b) Five
(c) Six (d) Eight
50. A photo diode can be used:
- (a) For detection of visible light (b) For detection of invisible light
(c) Both (a) and (b) (d) As an inductor
51. The diode used for the detection of visible and in visible light is:
- (a) Photodiode (b) Photo voltaic cell
(c) Light emitting (d) All of above
52. A diode, which can turn current ON and OFF in nanosecond is called:
- (a) Photo voltaic cell (b) Light emitting diode
(c) Photodiode (d) None of these
53. Photodiode is operated:
- (a) In the reversed biased situation (b) In the forward biased situation
(c) With the light incident upon it (d) Both (a) and (c)

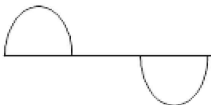54. Photo voltaic cell is also called:
- (a) Solar cell (b) Generator
(c) Thermo couple (d) Thermister
55. A single photovoltaic cell produces a current of:
- (a) 0.9v (b) 0.6v
(c) 0.5v (d) 6.0v
56. A single photo voltaic cell produces a current of:
- (a) A few mA (b) A few μ A
(c) A few ampere (d) 1A
57. The light emitting diode emits light when it is:
- (a) Reverse biased (b) Forward biased
(c) Both (a) and (b) (d) None of these
58. The specially designed semi conductor diodes used as indicator lamps in electronic circuits are:
- (a) The switch (b) The light emitting diode
(c) The photo diode (d) Solar cells
59. The specially designed semi-conductor used for as fast countings in electronic circuits is:
- (a) Photo diodes (b) Light emitting diode
(c) Photo voltaic cell (d) Solar cell
60. A combination of p-type and N-type substance give rise to:
- (a) P-N junction (b) N-N-junction
(c) P-P junction (d) None of the above
61. When p-type of p-n-junction connected to positive end and N-type of the junction connected to the negative terminal of battery then the junction is:
- (a) Reverse biased (b) Forward biased
(c) Neutral (d) None of these
62. If a reverse current of a reverse biased junction is increased to a maximum value then:
- (a) Diode junction may break down (b) Voltage drops to zero
(c) Voltage becomes maximum (d) None of these
63. The forward resistance of the p-n-junction is expressed as:
- (a) $r_f = \Delta v_f \times \Delta I_f$ (b) $r_f = \Delta v_f - \Delta I_f$
(c) $r_f = \frac{\Delta v_f}{\Delta I_f}$ (d) $r_f = \frac{\Delta I_f}{\Delta V_f}$
64. The semi conductor diode has the property of a:
- (a) Two way conduction (b) One way conduction
(c) Zero conduction (d) None of these

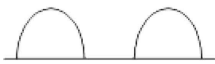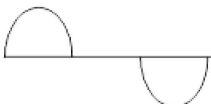65. If positive terminal of the battery is connected to n-type and negative terminal is connected to p-type then diode is:
- (a) Forward biased (b) Reverse biased
(c) Zero biased (d) Not biased
66. The process due to which current flows only during alternate half cycle is known as:
- (a) Half wave rectification (b) Full wave rectification
(c) Saturation (d) Amplification
67. The circuit of full wave rectification consist of:
- (a) Three diodes (b) Four diodes
(c) Two diodes (d) One diode
68. The wave form of an a.c voltage is:
- (a)  (b) 
(c)  (d) 
69. Which of the following diagram represents the wave form of an a.c voltage after full wave rectification:
- (a)  (b) 
(c)  (d) 
70. Which of the following diagram represents the wave form of a.c voltage after half wave rectification:
- (a)  (b) 
(c)  (d) 
71. Transistor was discovered by:
- (a) John Bardeen (b) I-carrie
(c) G Bell (d) Young
72. A transistor has:
- (a) Two region (b) One region
(c) Three region (d) Four region
73. In a certain circuit, $I_B = 40 \mu A$, $I_C = 20 \text{ mA}$:
- (a) 450 amp (b) 0.45 amp
(c) 5 m amp (d) 500 amp

74. The basic condition for a transistor amplifier circuit is:
- (a) The base-emitter junction should be forward biased
 - (b) The base-emitter junction should be reverse biased
 - (c) The base-collector junction should be forward biased
 - (d) None of these
75. Usually V_{BB} is:
- (a) Larger than V_{CC}
 - (b) Smaller than V_{CC}
 - (c) Equal to V_{CC}
 - (d) None of these
76. In order that a transistor acts as switch, a larger positive potential is applied across its:
- (a) Base-collector terminals
 - (b) Base emitter terminals
 - (c) Collector emitter terminals
 - (d) None of these
77. To turn the transistor OFF, the base current is set:
- (a) At zero value
 - (b) At maximum value
 - (c) At minimum value
 - (d) None of these
78. Types of transistors are:
- (a) Seven
 - (b) Two
 - (c) Four
 - (d) Three
79. In the transistor schematic symbol, the arrow is:
- (a) Located on the base
 - (b) Located on the collector
 - (c) Located on the emitter
 - (d) None of these
80. The term transistor stands for:
- (a) Transfer of resistance
 - (b) Transfer of current
 - (c) Transfer of charge
 - (d) Transfer of energy
81. The transistor in a circuit basically acts as:
- (a) Power amplifier
 - (b) Current amplifier
 - (c) Voltage amplifier
 - (d) None of these
82. Transistor can be used as:
- (a) Oscillator
 - (b) Switches
 - (c) Units
 - (d) All of above
83. When a transistor is used in a circuit generally:
- (a) The collector-base junction is forward biased and the collector-base junction is reverse biased
 - (b) Both the junctions are forward biased
 - (c) Both the junction are reverse biased
 - (d) None of these

84. The symbol of p-n-p transistor is:

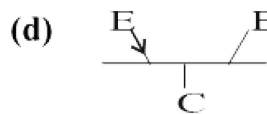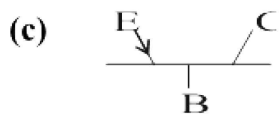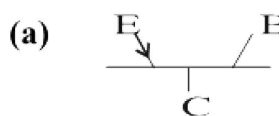

85. The characteristic of transistor are:

- | | |
|---------------------------|---------------------|
| (a) Temperature dependent | (b) Sound dependent |
| (c) Energy dependent | (d) Light dependent |

86. Emitter base junction is always:

- | | |
|------------------------------|--------------------|
| (a) Forward biased | (b) Reverse biased |
| (c) Both forward and reverse | (d) None of these |

87. The emitter and base has concentration of impurity:

- | | |
|-------------|-------------------|
| (a) Less | (b) Zero |
| (c) Greater | (d) None of these |

88. Identify which device used the rectification:

- | | |
|----------------|------------------|
| (a) Inductor | (b) Capacitor |
| (c) Transistor | (d) P-n junction |

89. Which one of the following device based on p-n junction:

- | | |
|------------------------|--------------------------|
| (a) Photo diode | (b) Light emitting diode |
| (c) Photo voltaic cell | (d) All of the above |

90. Light emitting diode based on:

- | |
|--|
| (a) Emission of energy in the form of photons |
| (b) Faradays law |
| (c) Ionic bonding between p-type and n-type substances |
| (d) None of these |

91. Photo diode can be used as:

- | | |
|-----------------------------------|------------------------|
| (a) A automatic ON and OFF switch | (b) Direction of light |
| (c) Logic gates | (d) All of above |

92. The central region of n-p-n transistor is known as:

- | | |
|-------------|-------------------|
| (a) Base | (b) Collector |
| (c) Emitter | (d) None of above |

93. In general, most of the electrical circuits make use of:

- | | |
|----------------------|----------------------|
| (a) n-n junction | (b) p-p junction |
| (c) n-p-n transistor | (d) p-n-p transistor |

94. For normal transistor the emitter current can be given by:
(a) $I_E = I_C$ (b) $I_E = I_C + I_B$
(c) $I_E = I_B$ (d) None of these
95. When light emitting diode is forward biased, it emits light of colour:
(a) Yellow (b) Green
(c) Red (d) All of the above
96. The advantage of LEDs is:
(a) High operating speed (b) Small size
(c) Reliability (d) All
97. In n-p-n transistor, the current flows in the direction from:
(a) Base to emitter (b) Collector to emitter
(c) Emitter to base (d) Base to collector
98. In p-n-p transistor, the current flows in the direction from:
(a) Base to emitter (b) Emitter to collector
(c) Emitter to base (d) Base to collector
99. In a transistor which one is very thin:
(a) Base (b) Collector
(c) Emitter (d) None of these
100. The thickness of the base is of the order of:
(a) 10^{-6} m (b) 10^{-4} m
(c) 10^{-2} m (d) 10^4 m
101. A transistor consists of three electrical contact which one of these is rectifying:
(a) Collector (b) Base
(c) Emitter (d) Both (a) and (c)
102. An expression for current gain of a transistor is given by:
(a) $\beta = \frac{I_B}{I_C}$ (b) $\beta = I_C + I_B$
(c) $\beta = I_C - I_B$ (d) $\beta = \frac{I_B}{I_C}$
103. When transistor works as an amplifier, its output is:
(a) Zero (b) Greater
(c) Less (d) Greater or less directly proportional to the input
104. An operational amplifier can be used as:
(a) Night switch (b) Comparator
(c) Inverting and non-inverting amplifier (d) All of the above

105. An operational amplifier have how many input terminals:
- (a) Two (b) Four
(c) Three (d) Five
106. An operational amplifier will act as inverting amplifier, when the input signal is connected to:
- (a) Earthed wire (b) Inverting terminal
(c) Non inverting terminal (d) None of these
107. The operational-amplifier is so called because it was some times used to perform mathematical operations:
- (a) Chemically (b) Electronically
(c) Electrically (d) Mechanically
108. An op-amp has input terminals namely:
- (a) Inverting (–) input (b) Non-inverting C+D
(c) Both (a) and (b) (d) None of these
109. The resistance between (+) and (–) inputs of an op-amp is of the order of:
- (a) Several mega ohms (b) A few ohms
(c) Both (a) and (b) (d) None of these
110. To use an op-amp as an inverting amplifier, the terminal which is grounded is the:
- (a) Inverting terminal (b) Non-inverting terminal
(c) Out put terminal (d) None of these
111. In case of op-amp as an inverting amplifier, $V_+ - V_- = 0$, this is because:
- (a) Open gain loop is very low (b) Closed loop gain is very high
(c) Open loop gain is very high (d) Both (a) and (a)
112. In order to use the op-amp as non-inverting amplifier, the input signal is applied as:
- (a) Non-inverting (+) terminal (b) Inverting (–) terminal
(c) Inverting (+) terminal (d) All of above
113. If $R_1 = 10 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, the gain of the op-amp acting as inverting amplifier comes out to be:
- (a) +10 (b) –10
(c) +0.1 (d) –0.1
114. The open loop gain of an op-amplifier is of the order of:
- (a) 10^3 (b) 10^4
(c) 10^6 (d) 10^5
115. The number of input terminals of an op-amplifier is:
- (a) Four (b) Two
(c) Three (d) One


116. Operational-amplifier has been discussed as comparator of:
- (a) Voltage (b) Current
(c) Displacement (d) Electric fields
117. The operational amplifier is:
- (a) A high gain amplifier (b) A high-power amplifier
(c) A high resistance amplifier (d) A low resistance amplifier
118. An op-amplifier can apply to:
- (a) A.C only (b) D.C only
(c) Both A.C and D.C (d) None of these
119. Non-inverting amplifier circuit have:
- (a) A very low input impedance (b) A very high input impedance
(c) A low output impedance (d) None of these
120. An expression for gain of an inverting amplifier is:
- (a) $-\frac{R_2}{R_1}$ (b) $\frac{R_1}{R_2}$
(c) $(R_1 R_2)$ (d) None of these
121. The value of open loop gain value for the amplifier is:
- (a) Zero (b) Infinity
(c) Very high (d) Very low
122. An expression for gain of non-inverting amplifier is:
- (a) $G = 1 + \frac{R_2}{R_1}$ (b) $G = 1 + \frac{R_1}{R_2}$
(c) $G = 1 - \frac{R_1}{R_2}$ (d) $G = 1 + R_1 R_2$
123. A system which deals with quantities or variables which have only two discrete values or states is known as:
- (a) Binary system (b) Logic gate
(c) Number system (d) Digital system
124. In describing functions of digital system, a lighted bulb will be described as:
- (a) Infinity (b) 1
(c) 0 (d) None of these
125. Which of the following is basic operation of Boolean algebra:
- (a) AND operation (b) NOT operation
(c) OR operation (d) All of these

126. A circuit which has two or more input signals that delivers an output when any one or more input signals are energetic is known as:
- (a) AND gate (b) OR gate
(c) NOT gate (d) NOR gate
127. A circuit which has two or more input signals and which delivers an output only when every input signal is energetic is known as:
- (a) OR gate (b) NOT gate
(c) AND gate (d) NOR gate
128. The logic circuit with one input and one output that inverts the input signal at the output is known as:
- (a) OR gate (b) NOT gate
(c) AND gate (d) NOR gate
129. The mathematical symbol for OR operation:
- (a) $X = A.B$ (b) $X = \overline{A} . \overline{B}$
(c) $X = A + B$ (d) $X = \overline{A + B}$
130. ♀ The mathematical symbol for AND gate is:
- (a) $X = \overline{A + B}$ (b) $X = A.B$
(c) $X = A + B$ (d) $X = \overline{A} . \overline{B}$
131. ♀ The mathematical symbol for NOR operation is:
- (a) $X = \overline{A + B}$ (b) $X = A.B$
(c) $X = A + D$ (d) $X = \overline{A} . \overline{B}$
132. ♀ The mathematical symbol for NAND operation is:
- (a) $X = A + B$ (b) $X = \overline{A} . \overline{B}$
(c) $X = \overline{A} . \overline{B}$ (d) $X = \overline{A + B}$
133. The logic gates are used in:
- (a) Pocket calculators (b) Robots
(c) Digital watches (d) All of these
134. In describing functions of digital system, 0 represents:
- (a) OFF (b) True
(c) ON (d) Lighted
135. In describing function of digital system, 1 represents:
- (a) True statement (b) Closed switch
(c) Lighted bulb (d) All of above

136. The values 1 and 0 are designated as:
- (a) Binary values
 - (b) Continuous values
 - (c) Decimal values
 - (d) None of these
137. The gate will recognize the voltage as high or 1 if the voltage applied to the gate is:
- (a) 1.5 volt
 - (b) 3.5 volt
 - (c) 0.5 volt
 - (d) 0.7 volt
138. The gate will recognize the voltage as 1 or 0 if the voltage applied to the gate is:
- (a) 3.5 volt
 - (b) 0.5 volt
 - (c) 5.5 volt
 - (d) 7.5 volt
139. In OR gate, the output is 1 if:
- (a) At least one input is 1
 - (b) Both inputs are 1
 - (c) Both inputs are 0
 - (d) None of these
140. In AND gate, the output is 0 if:
- (a) Both inputs are 1
 - (b) Both inputs are 0
 - (c) One input is Zero
 - (d) None of these
141. In AND gate, the output is 1 if:
- (a) Both inputs are 1
 - (b) Both inputs are 0
 - (c) One input is 0
 - (d) None of these
142. The gate, which performs the operation of inversion is called:
- (a) NOT gate
 - (b) AND gate
 - (c) OR gate
 - (d) XOR gate
143. The gate, which changes the logic level to its opposite level is called:
- (a) NOR gate
 - (b) AND gate
 - (c) OR gate
 - (d) NOT gate
144. If both the inputs given to a gate are 1, such that the output is 0 then it is:
- (a) NAND gate
 - (b) NOR gate
 - (c) XOR gate
 - (d) All of these
145. If both the inputs given to a gate are 0 such that the output is 1 then it is:
- (a) NAND gate
 - (b) NOR gate
 - (c) XN, OR gate
 - (d) All of these
146. XOR gate can be made by combining:
- (a) NOR, AND, NOT gates
 - (b) OR, AND, NOT gates
 - (c) OR, NAND, NOT gates
 - (d) OR, NOR, NOT gates

147. XNOR gate can be made by combining:
- (a) OR, NOR, NOT gate (b) OR, AND, NO gates
(c) OR, NAND, NOT gates (d) NOR, AND, NOT gates
148. At higher temperature, potential barrier voltage:
- (a) Decreases (b) Increases
(c) No change (d) None
149. Width of depletion region is:
- (a) 10^{-8} m (b) 10^{-7} m
(c) 10^{-6} m (d) 10^{-4} m
150. The barrier voltage is more for silicon because of its ——— atomic number allows more stability in covalent bonds.
- (a) High (b) Low
(c) Both (a), (b) (d) None
151. Breakdown voltage is:
- (a) 25 V (b) 15 V
(c) 35 V (d) 5 V
152. The value of reverse current for Ge is:
- (a) $1\ \mu\text{A}$ (b) 1 mA
(c) 1 A (d) 1 MA
153. Device used for conversion of D.C. to A.C. is:
- (a) Oscillator (b) Rectifier
(c) Amplifier (d) None
154. p-n junction when reversed biased acts as a:
- (a) Capacitor (b) On switch
(c) Off switch (d) None
155. Pulsating D.C. can be made smooth by using a circuit known as:
- (a) Filter (b) Tank
(c) Acceptor (d) All
156. A photodiode can switch its current on OR off in:
- (a) nano second (b) milli second
(c) micro second (d) centi second
157. Photodiode is used in:
- (a) Automatic switch (b) Optical communication equipment
(c) Light meters (d) All

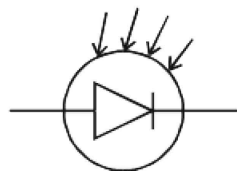158. Silicon transistors are preferred because:
- (a) High operating temperature (b) Low leakage current
(c) Suited to high frequency circuits (d) All
159. Current gain of a transistor which has collector current of 10 mA and a base current of $40\ \mu\text{A}$ is:
- (a) 25 (b) 250
(c) 2500 (d) 25000
160. In case of common emitter amplifier, phase difference between input and out:
- (a) 0° (b) 120°
(c) 180° (d) 90°
161. When transistor acts as OFF switch then voltage across collector and emitter is _____ V_{CC} .
- (a) Less than (b) Greater than
(c) Equal to (d) None
162. LDR is a:
- (a) Conductor (b) Semiconductor
(c) Insulator (d) None
163. During day time, when light is falling upon LDR, R_L is:
- (a) Large (b) Unchanged
(c) Small (d) None
164. The photovoltaic cell is always:
- (a) Forward biased (b) Reverse biased
(c) No biasing is required (d) None
165. Under ideal conditions, the collector current is:
- (a) Equal to base current (b) Nearly equal to emitter current
(c) Less than base current (d) Always zero



166. The symbol ————— represents:

- (a) LED (b) Photodiode
(c) Diode (d) All
167. One use of a single p-n junction semiconductor in an electrical circuit is a:
- (a) Rectifier (b) Transistor
(c) Battery (d) Diode
168. The main difference between intrinsic and extrinsic semiconductor, under ambient condition, is:
- (a) Shape (b) Density
(c) Electrons (d) Resistivity

169. The output from a full wave rectifier is.
- (a) An ac voltage
 - (b) A dc voltage
 - (c) Zero
 - (d) A pulsating unidirectional voltage
170. A piece of copper and another of germanium are cooled from room temperature to 80K. The resistance of:
- (a) Each of them increases
 - (b) Each of them decreases
 - (c) Copper increases and that of germanium decreases
 - (d) Copper decreases and that of germanium increases
171. The electrical conductivity of a semiconductor increases if electromagnetic radiation of wavelength shorter than 2066 nm is incident on it. The band gap energy (in eV) for the semiconductor is very nearly equal to.
- (a) 0.5
 - (b) 0.6
 - (c) 0.8
 - (d) 1.2

ANSWERS

1.	(b)	2.	(b)	3.	(b)	4.	(c)	5.	(a)
6.	(d)	7.	(a)	8.	(b)	9.	(c)	10.	(a)
11.	(c)	12.	(b)	13.	(a)	14.	(c)	15.	(a)
16.	(d)	17.	(c)	18.	(a)	19.	(c)	20.	(c)
21.	(c)	22.	(c)	23.	(b)	24.	(c)	25.	(b)
26.	(a)	27.	(d)	28.	(b)	29.	(a)	30.	(c)
31.	(a)	32.	(d)	33.	(b)	34.	(d)	35.	(b)
36.	(c)	37.	(d)	38.	(a)	39.	(b)	40.	(b)
41.	(a)	42.	(c)	43.	(d)	44.	(a)	45.	(c)
46.	(a)	47.	(d)	48.	(c)	49.	(a)	50.	(c)
51.	(a)	52.	(c)	53.	(d)	54.	(a)	55.	(b)
56.	(a)	57.	(b)	58.	(b)	59.	(a)	60.	(a)
61.	(b)	62.	(a)	63.	(c)	64.	(b)	65.	(b)
66.	(a)	67.	(b)	68.	(c)	69.	(b)	70.	(c)
71.	(a)	72.	(c)	73.	(d)	74.	(a)	75.	(a)
76.	(b)	77.	(a)	78.	(b)	79.	(c)	80.	(a)
81.	(b)	82.	(d)	83.	(a)	84.	(c)	85.	(a)
86.	(a)	87.	(c)	88.	(d)	89.	(d)	90.	(a)
91.	(d)	92.	(a)	93.	(c)	94.	(b)	95.	(d)
96.	(d)	97.	(a)	98.	(c)	99.	(a)	100.	(a)
101.	(d)	102.	(d)	103.	(d)	104.	(d)	105.	(a)
106.	(c)	107.	(b)	108.	(c)	109.	(a)	110.	(b)
111.	(c)	112.	(a)	113.	(b)	114.	(d)	115.	(b)
116.	(a)	117.	(a)	118.	(a)	119.	(b)	120.	(a)
121.	(c)	122.	(a)	123.	(b)	124.	(b)	125.	(a)
126.	(b)	127.	(c)	128.	(b)	129.	(c)	130.	(b)
131.	(a)	132.	(b)	133.	(d)	134.	(a)	135.	(d)
136.	(a)	137.	(b)	138.	(b)	139.	(a)	140.	(b)
141.	(a)	142.	(a)	143.	(d)	144.	(d)	145.	(d)
146.	(b)	147.	(d)	148.	(a)	149.	(c)	150.	(b)
151.	(a)	152.	(b)	153.	(a)	154.	(c)	155.	(a)
156.	(a)	157.	(d)	158.	(d)	159.	(b)	160.	(c)
161.	(c)	162.	(b)	163.	(c)	164.	(c)	165.	(b)
166.	(b)	167.	(a)	168.	(d)	169.	(d)	170.	(d)
171.	(c)								